

**CS2022: 數位系統設計**

**Memory and Programmable Logic**

---

# Outline

---

- ▣ Introduction
- ▣ Random-Access Memory
- ▣ Memory Decoding
- ▣ Error Detection and Correction
- ▣ Read-Only Memory
- ▣ Programmable Logic Array
- ▣ Programmable Array Logic
- ▣ Sequential Programmable Devices

# Introduction

## ■ Memory

- ◆ Information storage
- ◆ A collection of cells store binary information

## ■ RAM – Random-Access Memory

- ◆ Read operation
- ◆ Write operation


## ■ ROM – Read-Only Memory

- ◆ Read operation only
- ◆ A programmable logic device


# Programmable Logic Device
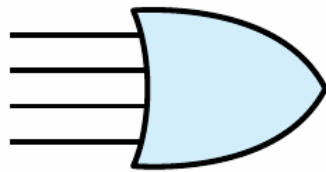
## ■ Programmable Logic Device (PLD)

- ◆ ROM – read only memory
- ◆ PLA – programmable logic array
- ◆ PAL – programmable array logic
- ◆ FPGA – field-programmable gate array
  - » programmable logic blocks
  - » programmable interconnects



(a) Conventional symbol

 

(b) Array logic symbol

Fig. 1 Conventional and array logic diagrams for OR gates

# Random-Access Memory

## ■ A memory unit

- ◆ Stores binary information in groups of bits (words)
- ◆ 8 bits (1 byte), 2 bytes, 4 bytes

## ■ Block diagram

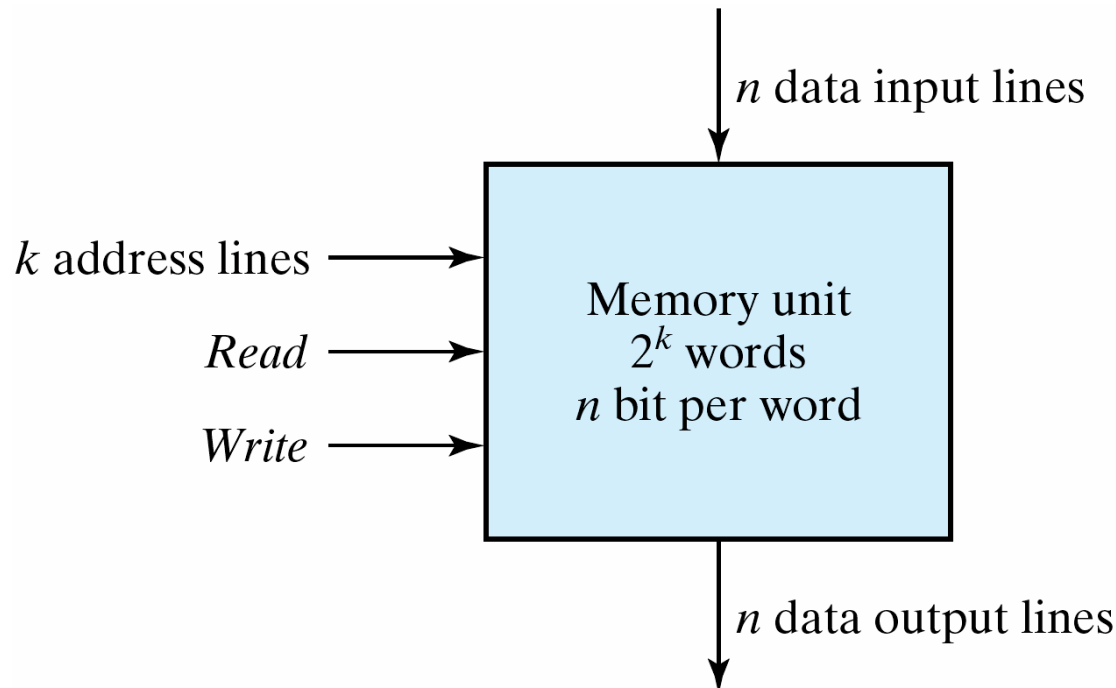


Fig. 2 Block diagrams of a memory unit

# Example: 1024 × 16 Memory

Memory address		Memory content
Binary	Decimal	
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101

Fig. 3 Contents of a 1024 × 16 memory

# Write and Read Operations

## ■ Write operation

- Apply the binary address to the address lines
- Apply the data bits to the data input lines
- Activate the *write* input

## ■ Read operation

- Apply the binary address to the address lines
- Activate the *read* input

**Table 7.1**

*Control Inputs to Memory Chip*

Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word


# Timing Waveforms

- ▣ The operation of the memory unit is controlled by an external device
- ▣ The memory **access time**
  - ◆ the time required to select a word and **read** it
- ▣ The memory **cycle time**
  - ◆ the time required to complete a **write** operation
- ▣ Read and write operations must be synchronized with a clock
  - ◆ Usually, CPU clock cycle time < memory access/cycle time
  - ◆ Multiple CPU clock cycles for a memory operation


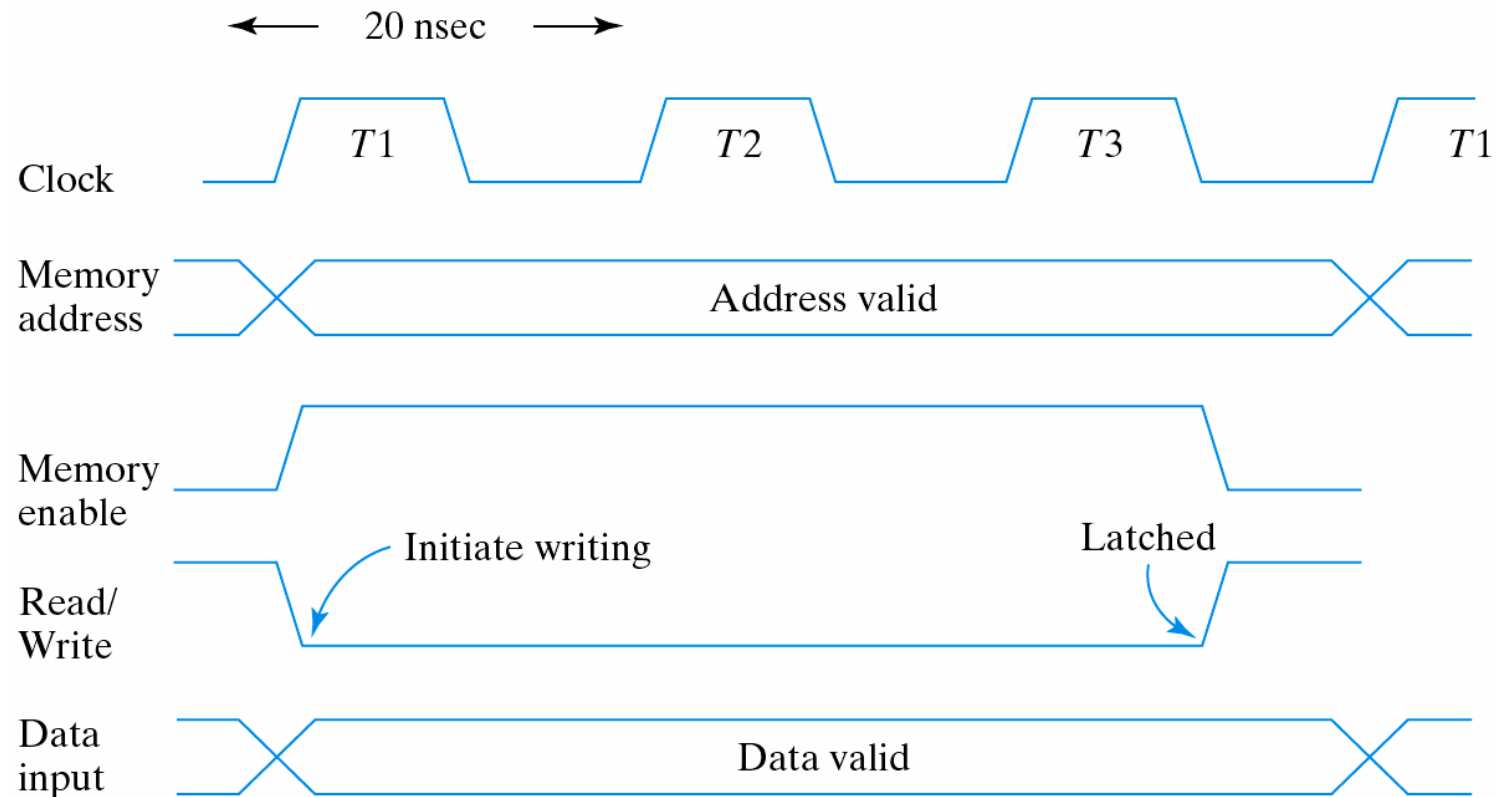
# Memory Write Cycle


- ◆ Assume that CPU clock: 50 MHz (i.e., cycle time = 20 ns)
- ◆ Memory access/cycle time < 50 ns



(a) Write cycle

Fig. 4 Memory cycle timing waveforms

# Memory Read Cycle

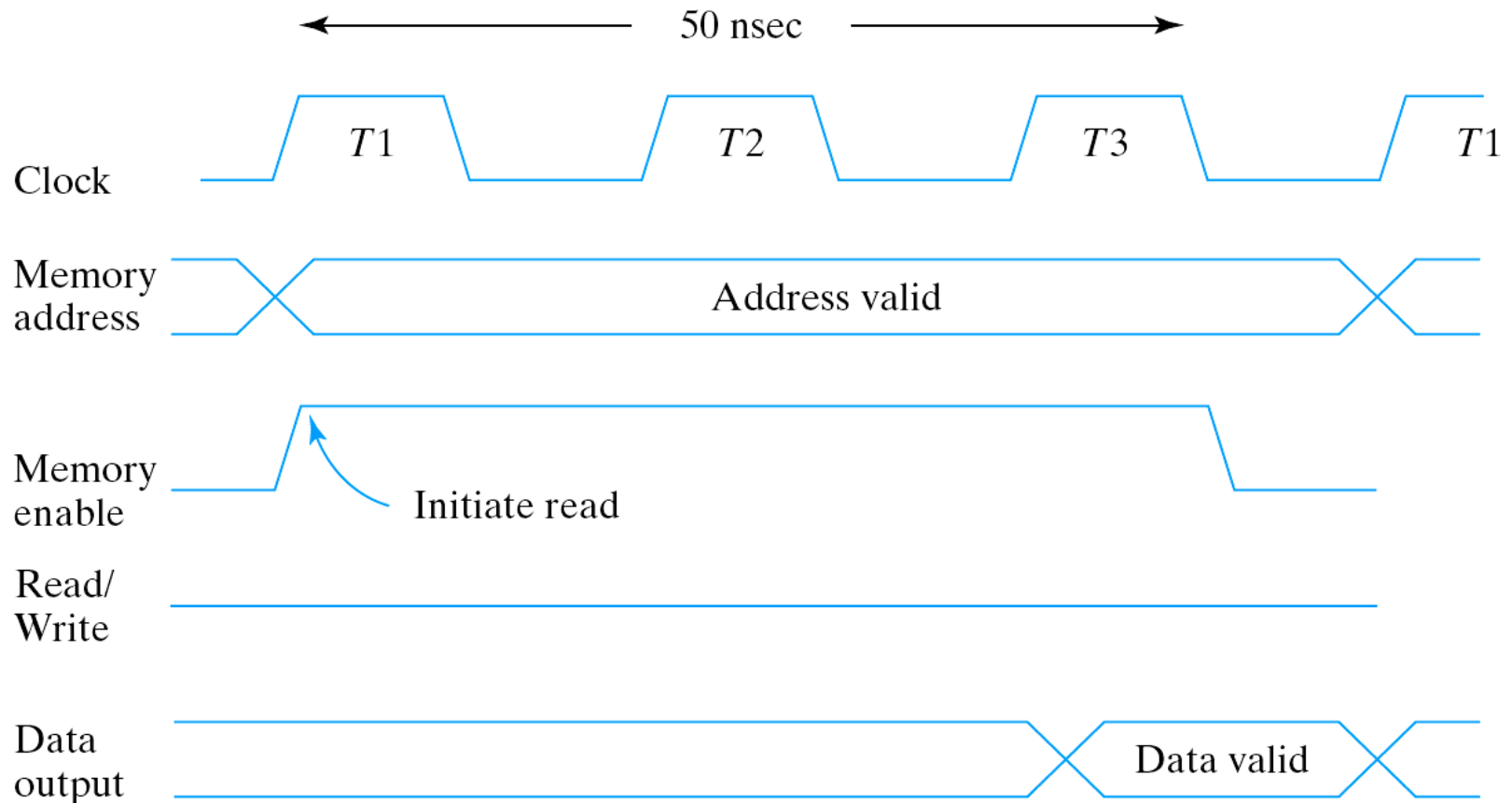

(b) Read cycle

Fig. 4 Memory cycle timing waveforms

# Types of Memories (1/2)

## ■ Random-access memory – RAM

- ◆ Access time is the same regardless the data location
- ◆ Cp.: hard disk, CD-ROM, DVD-ROM, tape (sequential access)





## ■ Static memory – SRAM

- ◆ Information is stored in latches
- ◆ Remains valid as long as power is applied
- ◆ Short read/write cycle

## ■ Dynamic memory – DRAM




- ◆ Information are stored in the form of charges on capacitors
- ◆ The stored charge tends to discharge with time
- ◆ Need to be **refreshed** (read and write back)
- ◆ Reduced power consumption
- ◆ Larger memory capacity

# DRAM Cell

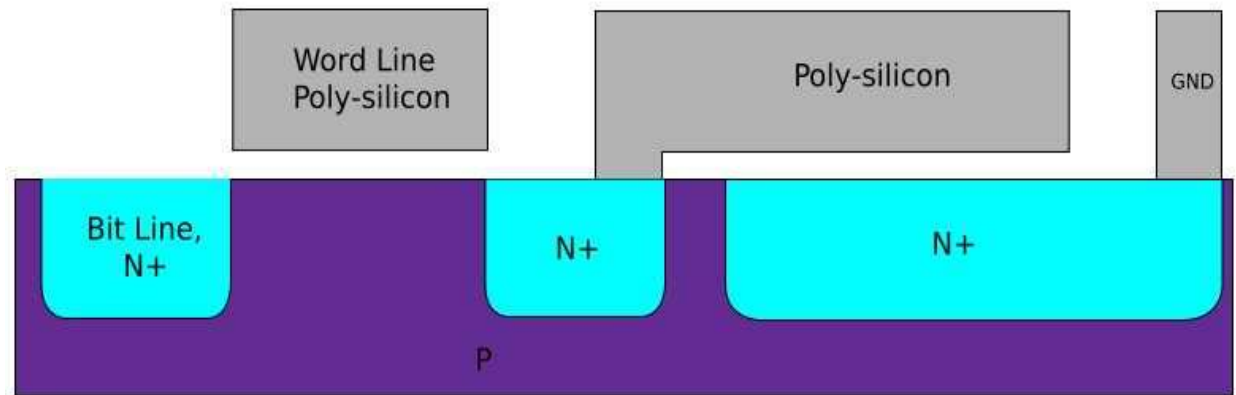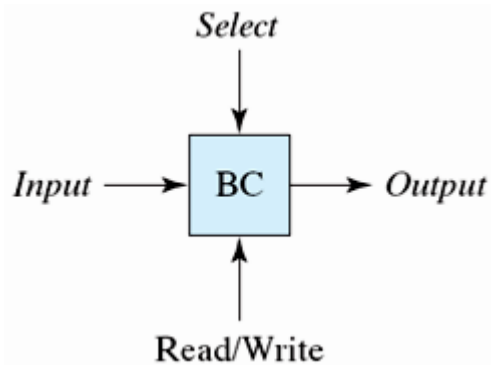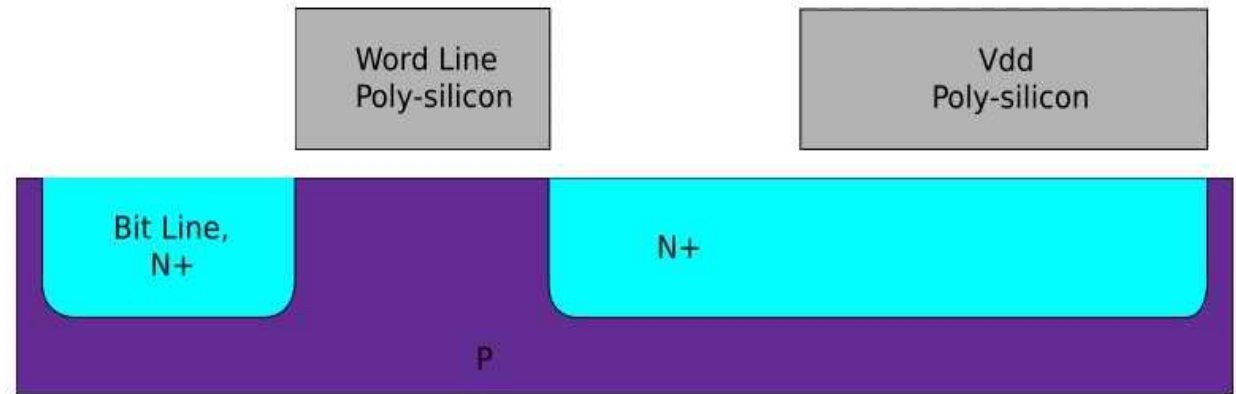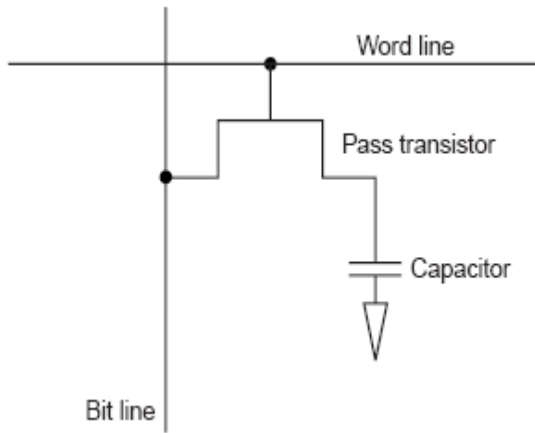

**Source: Wikipedia**

# SRAM Cell

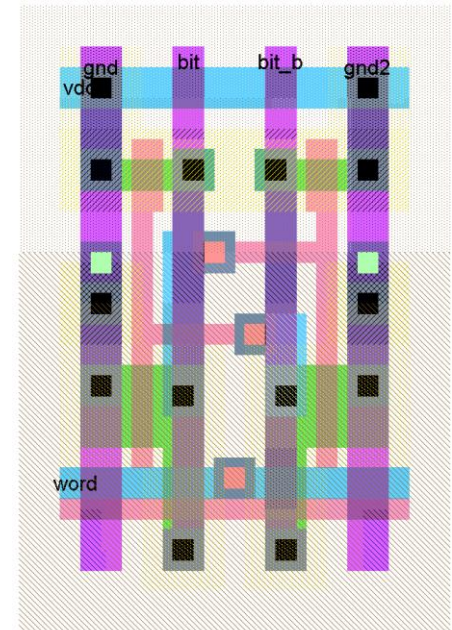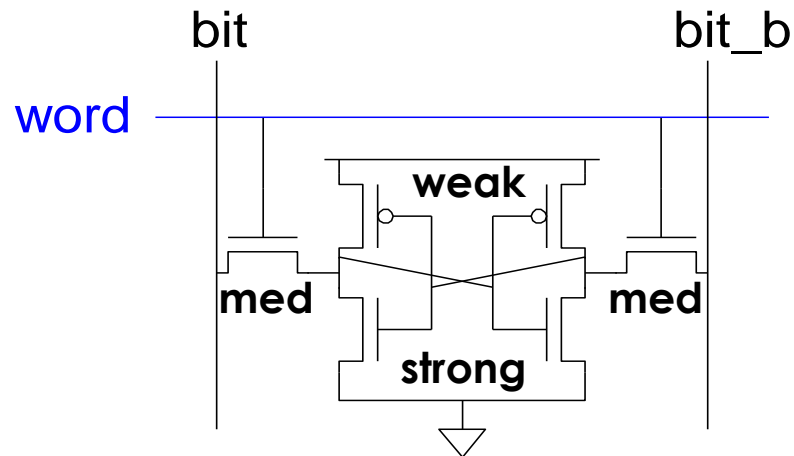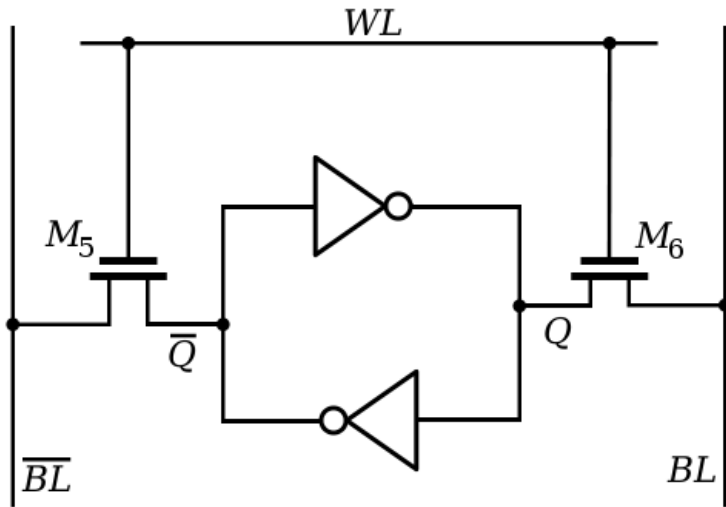

# Types of Memories (2/2)

## ▣ Volatile

- ◆ Lose stored information when power is turned off
- ◆ SRAM, DRAM


## ▣ Non-volatile

- ◆ Retains its stored information after the removal of power
- ◆ ROM
- ◆ EPROM, EEPROM
- ◆ Flash memory


# Memory Decoding
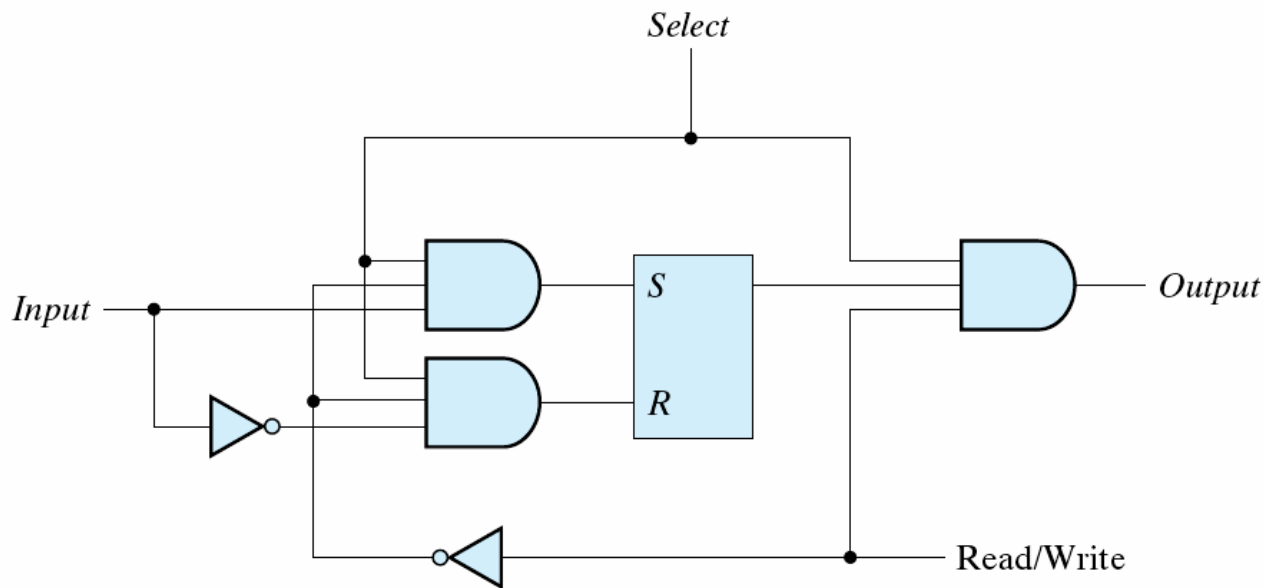
## ■ A memory unit

- ◆ The storage components
- ◆ The decoding circuits to select the memory word



(a) Logic diagram

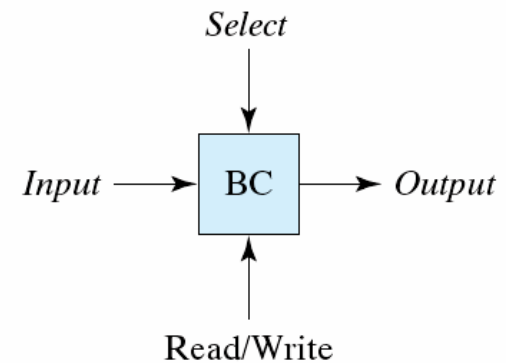

(b) Block diagram

Fig. 5 Memory cell (equivalent logic)

# Internal Construction

- A RAM of  $m$  words and  $n$  bits per word
  - ◆  $m \times n$  binary storage cells
  - ◆ Decoding circuits to select individual words
    - »  $k$ -to- $2^k$  decoder

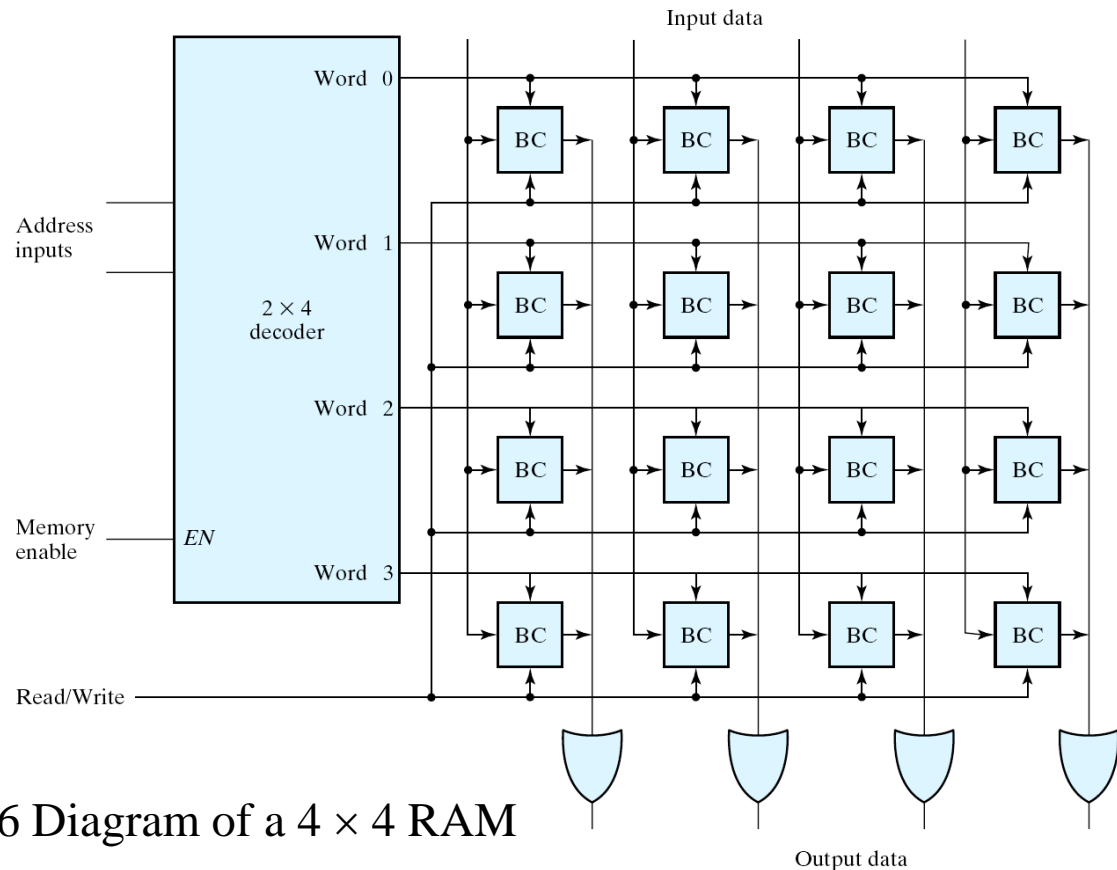


Fig. 6 Diagram of a 4 × 4 RAM



# Coincident Decoding (1/2)

- **A two-dimensional selection scheme**
  - ◆ Reduce the complexity of the decoding circuits
  
- **A 10-to-1024 decoder**
  - ◆ 1024 AND gates with 10 inputs per gates
  - ◆ Two 5-to-32 decoders
    - »  $2 * (32 \text{ AND gates with 5 inputs per gates})$
  - ◆ Reduce the circuit complexity and the cycle time

# Coincident Decoding (2/2)

 


Fig. 7 Two-dimensional decoding structure for a 1K-word memory

# Address Multiplexing (1/2)

- To reduce the number of pins in the IC package
  - ◆ consider a 64K×1 DRAM
    - » 16-bit address lines
  - ◆ Multiplex the address lines in one set of address input pins
    - » RAS: 8-bit row address strobe
    - » CAS: 8-bit column address strobe

# Address Multiplexing (2/2)

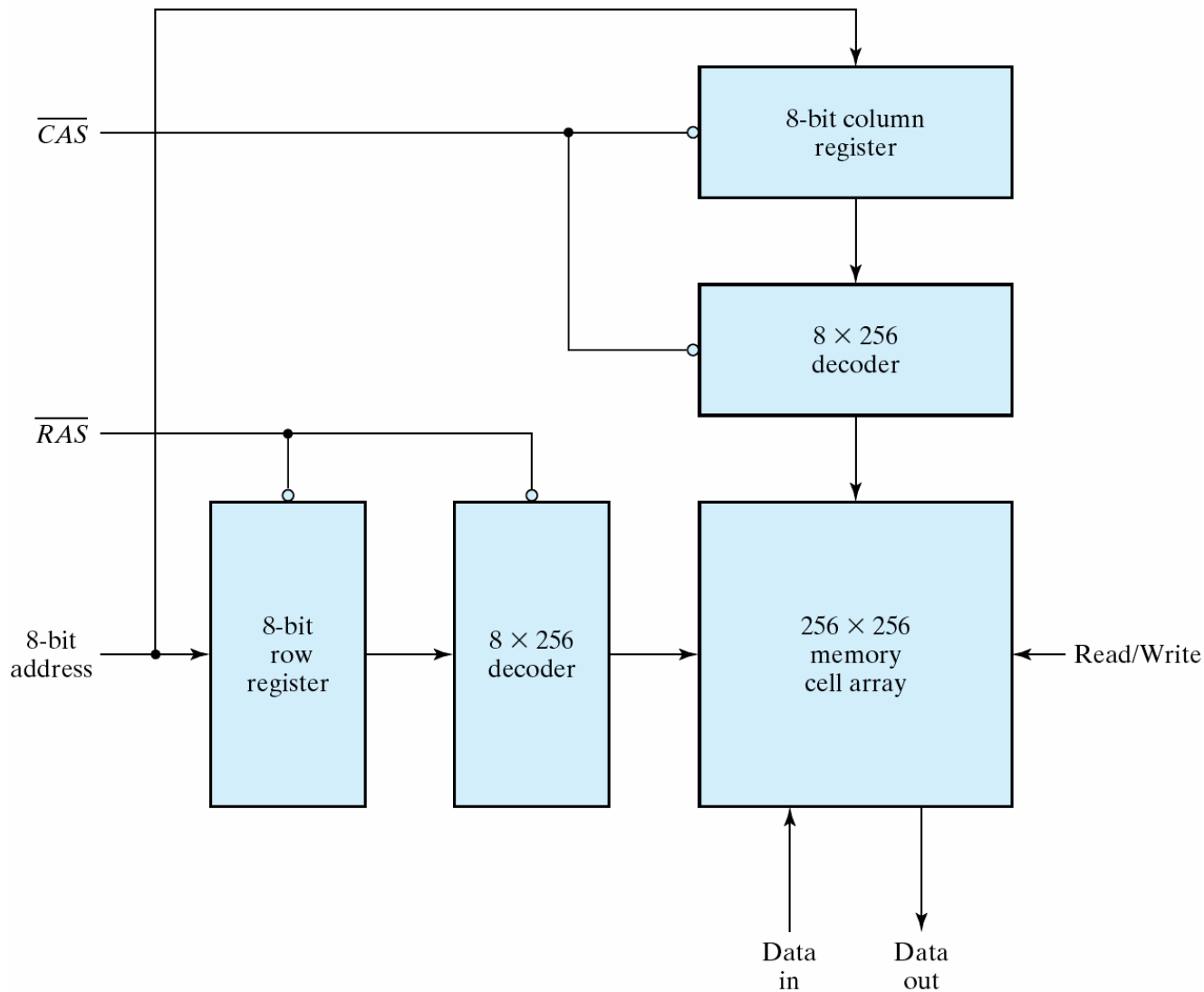


Fig. 8 Address multiplexing for a 64K DRAM

# Read-Only Memory

- ▣ Store permanent binary information

- ▣  $2^k \times n$  ROM

- ◆  $k$  address input lines
- ◆ Enable input(s)
- ◆ Three-state outputs

 


Fig. 9 ROM block diagram

# Internal Logic of a 32×8 ROM

- ◆ 5-to-32 decoder
- ◆ 8 OR gates
  - » Each has 32 inputs
- ◆ 32×8 internal programmable connections

 


Fig. 10 Internal logic of a 32 × 8 ROM  
Memory and Programmable Logic-32


# Programming a ROM

## □ Programmable interconnections

- ◆ Crosspoint switch
  - » Each "fuse" can be blown by applying a high voltage pulse
- ◆ Close (two lines are connected)
- ◆ Open (two lines are disconnected)

Table 7.3  
ROM Truth Table (Partial)

Inputs					Outputs							
$I_4$	$I_3$	$I_2$	$I_1$	$I_0$	$A_7$	$A_6$	$A_5$	$A_4$	$A_3$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		⋮						⋮				
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

 

# Combinational Circuit Implementation

## ▣ ROM: a decoder + OR gates

- ◆ Boolean function = sum of minterms
- ◆ For an  $n$ -input,  $m$ -output combinational circuit  
 $\Rightarrow 2^n \times m$  ROM

## ▣ Design procedure:

1. Determine the **size of ROM**
2. Obtain the programming **truth table** of the ROM
3. The truth table = the **fuse** pattern



# Three-Bit Binary Square (1/2)


**Table 7.4**

*Truth Table for Circuit of Example 7.1*

Inputs			Outputs						Decimal
$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$	$B_1$	$B_0$	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

- ◆ 3 inputs, 6 outputs
- ◆  $B_1 = 0$
- ◆  $B_0 = A_0$
- ◆ Use 8x4 ROM

# Three-Bit Binary Square (2/2)

 


(a) Block diagram

$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

(b) ROM truth table

Fig. 12 ROM implementation of Example 1

 

# Types of ROMs


## ▣ Types of ROM

- ◆ Mask programming ROM
  - » IC manufacturers, economical only if large quantities
- ◆ PROM: Programmable ROM
  - » Fuses, one-time program
- ◆ EPROM: erasable PROM
  - » Floating gate
  - » Ultraviolet light erasable
- ◆ EEPROM: electrically erasable PROM
  - » E<sup>2</sup>PROM
- ◆ Flash ROM
  - » Widespread applications in recent years
  - » Limited times of write operations  $\sim 10^5$  erase cycles


# Combinational PLDs

## ■ Three major types of combinational PLD


### ◆ AND-OR array

 

(a) Programmable read-only memory (PROM)

 

(b) Programmable array logic (PAL)

 

(c) Programmable logic array (PLA)

Fig. 13 Basic configuration of three PLDs

# Programmable Logic Array


## ■ Programmable Logic Array – PLA

- ◆ An array of programmable AND gates
  - » Capable of generating any product term
- ◆ An array of programmable OR gates
  - » Capable of generating sum of the products
- ◆ XOR gate at the output
  - » Capable of generating positive and negative phases
- ◆ More flexible than ROM
- ◆ Use less circuits than ROM
  - » Generate required product terms

# PLA Implementation (1/2)

$$F_1 = AB' + AC + A'BC'$$

$$F_2 = (AC + BC)'$$

 

**Table 7.5**  
*PLA Programming Table*

		Inputs			Outputs (T) (C)	
		A	B	C	$F_1$	$F_2$
$AB'$	1	1	0	—	1	—
$AC$	2	1	—	1	1	1
$BC$	3	—	1	1	—	1
$A'BC'$	4	0	1	0	1	—

Note: See text for meanings of dashes.

# PLA Implementation (2/2)

## ■ The size of a PLA

- ◆ The number of inputs
- ◆ The number of product terms (AND gates)
- ◆ The number of outputs (OR gates)

## ■ PLA design issues

- ◆ Reduce the number of distinct product terms
- ◆ The number of literals in a product is not important

# Examples 2 (1/2)

■  $F_1(A, B, C) = \Sigma (0, 1, 2, 4)$

■  $F_2(A, B, C) = \Sigma (0, 5, 6, 7)$

- ◆ Both the true value and the complement of the function should be simplified to check

$A \backslash BC$		$B$			
		00	01	11	10
$A$	0	$m_0$ 1	$m_1$ 1	$m_3$ 0	$m_2$ 1
	1	$m_4$ 1	$m_5$ 0	$m_7$ 0	$m_6$ 0

$A \backslash BC$		$B$			
		00	01	11	10
$A$	0	$m_0$ 1	$m_1$ 0	$m_3$ 0	$m_2$ 0
	1	$m_4$ 0	$m_5$ 1	$m_7$ 1	$m_6$ 1

Fig. 15 Solution to Example 2




# Examples 2 (2/2)

■  $F_1 = (AB + AC + BC)'$

■  $F_2 = AB + AC + A'B'C'$

PLA programming table

Product term		Inputs			Outputs	
		A	B	C	(C) $F_1$	(T) $F_2$
$AB$	1	1	1	–	1	1
$AC$	2	1	–	1	1	1
$BC$	3	–	1	1	1	–
$A'B'C'$	4	0	0	0	–	1

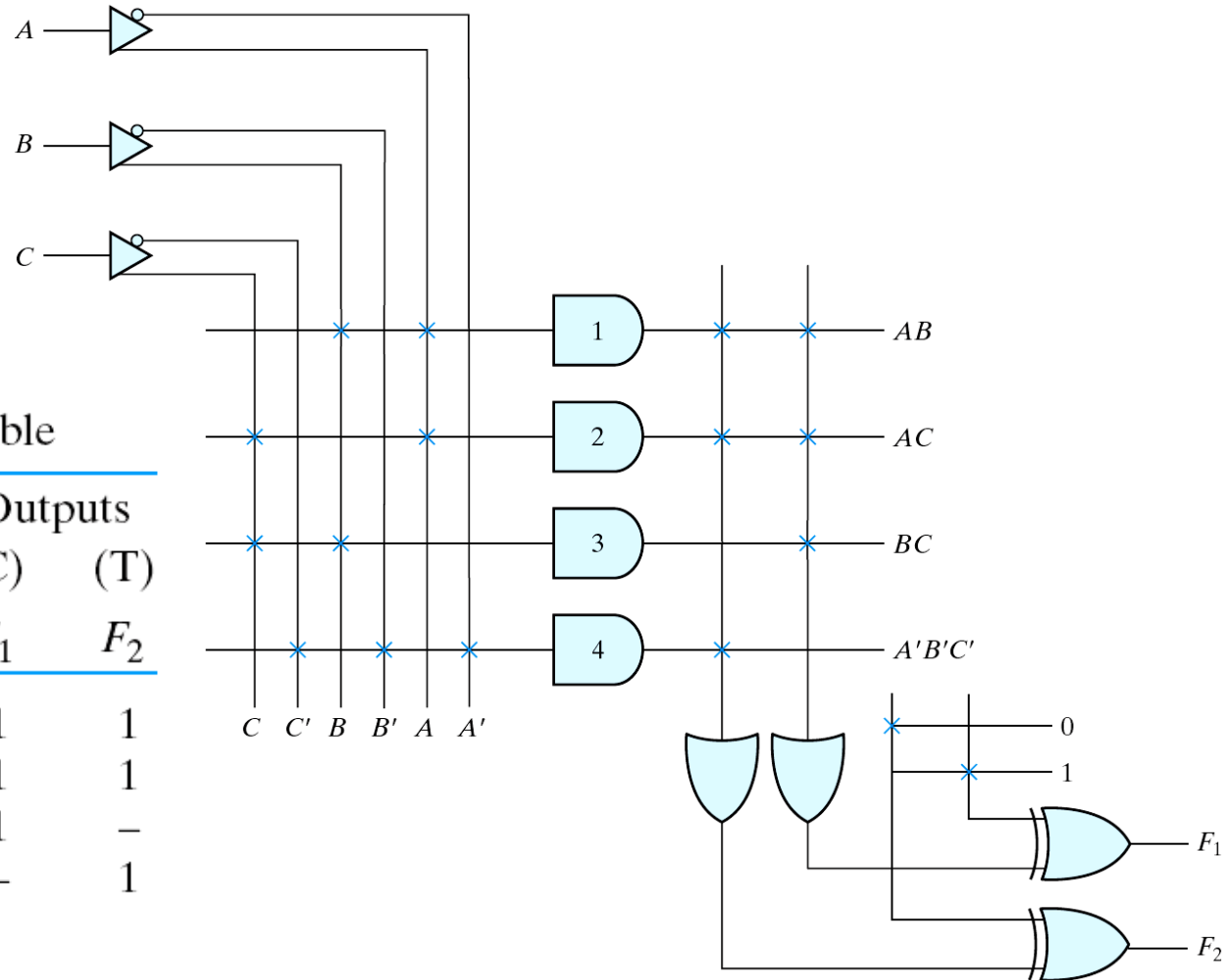

# Sequential Programmable Devices

## ▣ Sequential programmable logic device

- ◆ SPLD
- ◆ PLD + flip-flops

 


Fig. 18 Sequential programmable logic device

# Complex PLD

## ■ Complex PLD – CPLD

- ◆ Put a lot of PLDS on a chip
- ◆ Add wires between them whose connections can be programmed
- ◆ Use fuse/EEPROM technology


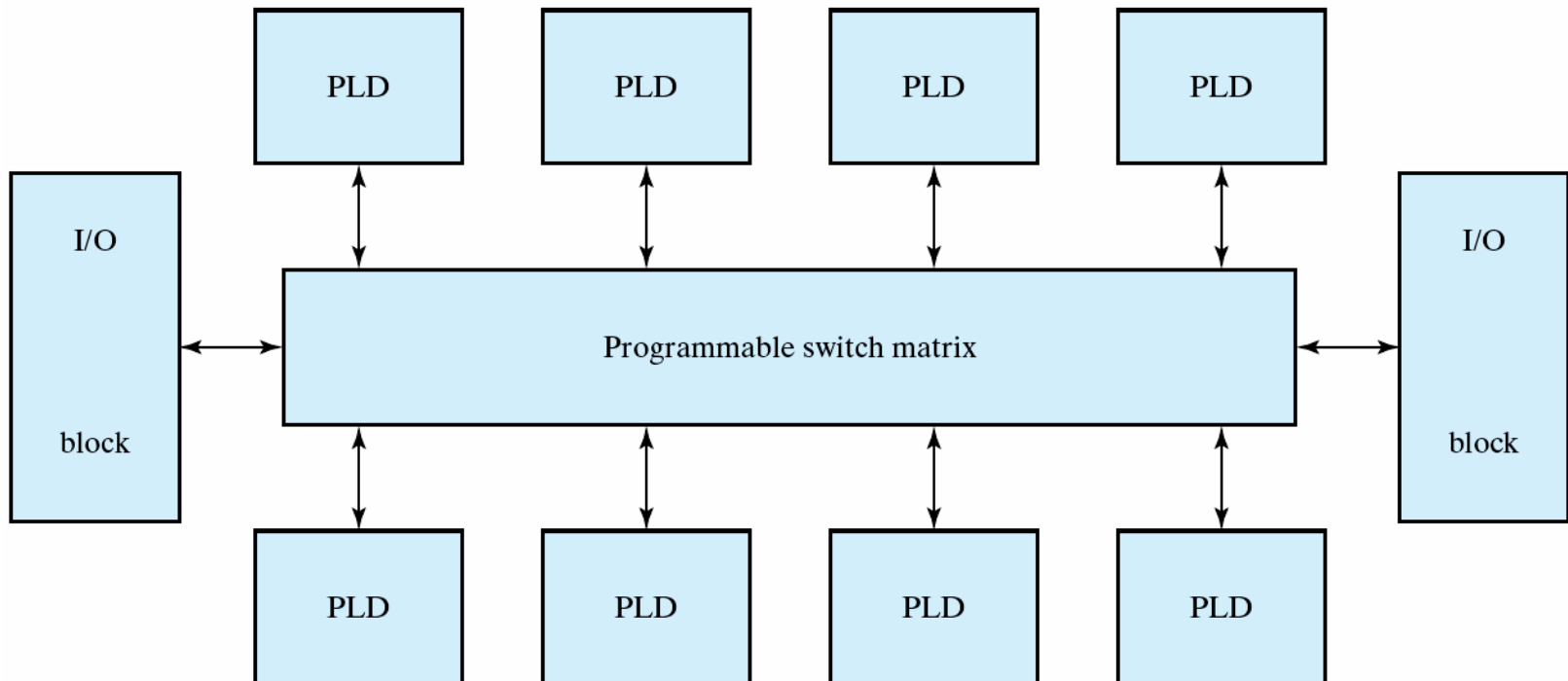


Fig. 20 General CPLD configuration  
Memory and Programmable Logic-53

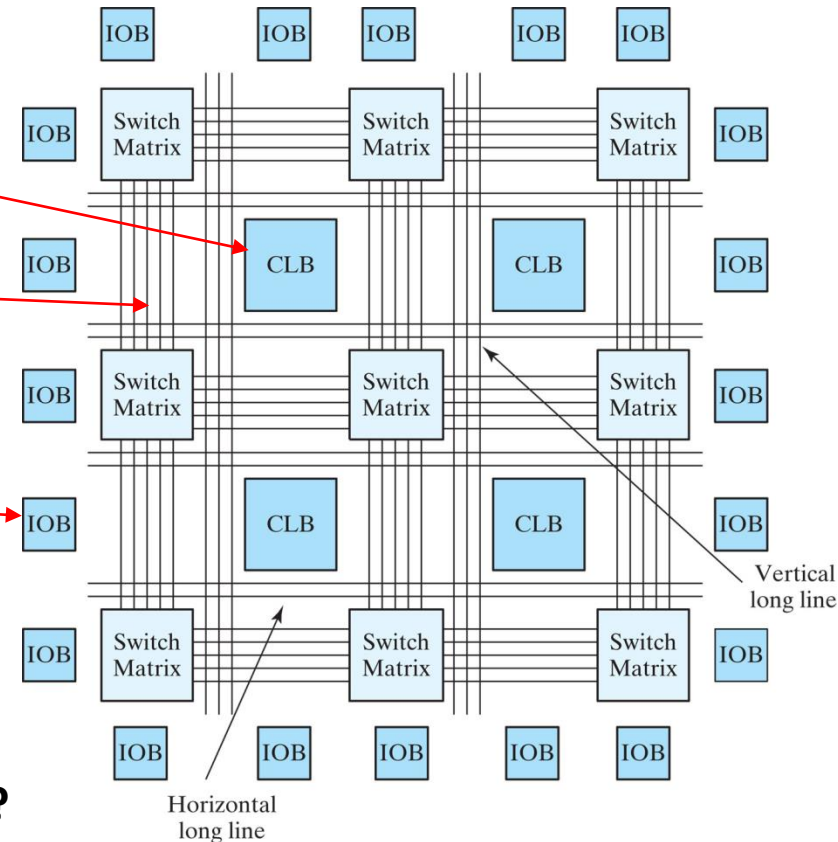
# Field-Programmable Gate Arrays

- **Logic blocks**
  - ◆ To implement combinational and sequential logic
- **Interconnect**
  - ◆ Wires to connect inputs and outputs to logic blocks
- **I/O blocks**
  - ◆ Special logic blocks at periphery of device for external connections
- **Key questions**
  - ◆ How to make logic blocks programmable?
  - ◆ How to connect the wires?



 
# Digital Systems

- ▣ Finite primitive elements create almost infinite possibilities!
- ◆ Enabling technology for almost EVERYTHING we take for granted today!





# Farewell & Happy New Year

 

羅賽塔和菲萊的彗星大冒險

[https://www.youtube.com/playlist?list=PLzYYnhQlXmVGDAJ9Dmn7V\\_alS5VBpZvMp](https://www.youtube.com/playlist?list=PLzYYnhQlXmVGDAJ9Dmn7V_alS5VBpZvMp)

We thank you for pushing the frontiers of knowledge for the advancement of humanity. ☺